

Surname											Other Names										
Centre Number											Candidate Number										
Candidate Signature																					

For Examiner's Use

General Certificate of Education
June 2008
Advanced Subsidiary Examination



ELECTRONICS
Unit 1 Foundation Electronics

ELE1

Friday 16 May 2008 9.00 am to 10.30 am

For this paper you must have:

- a pencil and a ruler
- a calculator.

Time allowed: 1 hour 30 minutes

Instructions

- Use black ink or black ball-point pen. Use pencil only for drawing.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Answers written in margins or on blank pages will not be marked.
- Do all rough work in this book. Cross through any work you do not want to be marked.
- A *Data Sheet* is provided on pages 3 and 4. Detach this perforated sheet at the start of the examination.

Information

- The maximum mark for this paper is 72.
- The marks for questions are shown in brackets.
- You are expected to use a calculator where appropriate.
- You are reminded of the need for good English and clear presentation in your answers.

For Examiner's Use			
Question	Mark	Question	Mark
1		5	
2		6	
3			
4			
Total (Column 1) —————→			
Total (Column 2) —————→			
TOTAL			
Examiner's Initials			



Data Sheet

- A perforated *Data Sheet* is provided as pages 3 and 4 of this question paper.
- This sheet may be useful for answering some of the questions in the examination.
- You may wish to detach this sheet before you begin work.




Data Sheet

Resistors Preferred values for resistors (E24) series:
1.0, 1.1, 1.2, 1.3, 1.5, 1.6, 1.8, 2.0, 2.2, 2.4, 2.7, 3.0, 3.3, 3.6, 3.9, 4.3,
4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1 ohms and multiples that are ten
times greater.

Resistor Printed Code (BS 1852) This code consists of letters and numbers:
R means $\times 1$
K means $\times 1000$ (i.e. 10^3)
M means $\times 1\,000\,000$ (i.e. 10^6)
Position of the letter gives the decimal point
Tolerances are given by the letter at the end of the code, F = $\pm 1\%$,
G = $\pm 2\%$, J = $\pm 5\%$, K = $\pm 10\%$, M = $\pm 20\%$.

Resistor Colour Code	Number	Colour
	0	Black
	1	Brown
	2	Red
	3	Orange
	4	Yellow
	5	Green
	6	Blue
	7	Violet
	8	Grey
	9	White

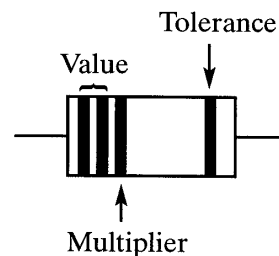Tolerance, gold = $\pm 5\%$, silver = $\pm 10\%$, no band $\pm 20\%$.



Silicon diode $V_F = 0.7\text{ V}$

Silicon transistor $V_{be} \approx 0.7\text{ V}$ in the on state
 $V_{ce} \approx 0.2\text{ V}$ when saturated

Resistance $R_T = R_1 + R_2 + R_3$ series
 $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ parallel

Capacitance $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ series
 $C_T = C_1 + C_2 + C_3$ parallel

Time constant $T = CR$

A.C. theory $I_{\text{rms}} = \frac{I_o}{\sqrt{2}}$

$$V_{\text{rms}} = \frac{V_o}{\sqrt{2}}$$

$X_C = \frac{1}{2\pi fC}$ reactance

$X_L = 2\pi fL$ reactance


$f = \frac{1}{T}$ frequency, period

$f_o = \frac{1}{2\pi\sqrt{LC}}$ resonant frequency



Answer **all** questions in the spaces provided.

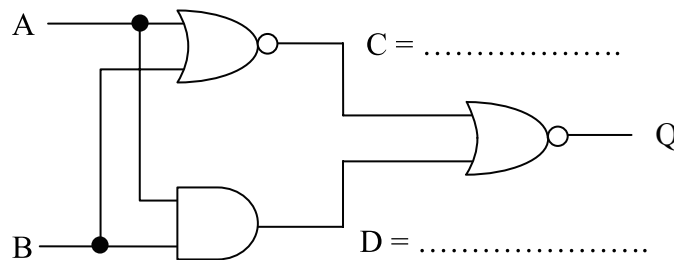- 1 A logic circuit diagram is shown below.



- 1 (a) Write the simplest Boolean expressions for the logic signals at points C and D on the diagram above in the spaces provided. (2 marks)

- 1 (b) (i) Write the simplest Boolean expression for Q in terms of C and D only.

Q =

- 1 (b) (ii) Write a simple Boolean expression for Q in terms of A and B only.

Q =

(3 marks)

- 1 (c) Complete the truth table to show the logic values of C, D and Q for all the combinations of variables A and B.

A	B	C	D	Q
0	0			
0	1			
1	0			
1	1			


(4 marks)

- 1 (d) Draw a logic circuit diagram in the space below using a single logic gate that would have the same function as the original circuit.

(2 marks)

Turn over ►

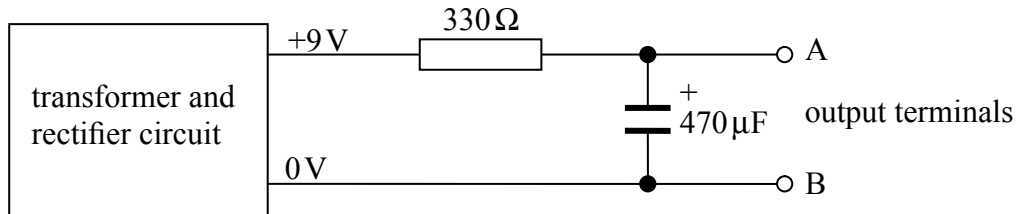2 The output stage of a power supply is shown below.



2 (a) (i) Calculate the current through the resistor when the output terminals are connected together.

.....

2 (a) (ii) Calculate the power dissipation of the resistor at this current.

.....

(4 marks)

2 (b) (i) Calculate the time constant of this circuit, assuming no load is connected to its output.

.....

2 (b) (ii) The 9 V supply is switched on and the capacitor is initially uncharged. Approximately how long will it take for the output voltage to reach 9 V?

.....

2 (b) (iii) A load resistance of 10 kΩ is connected between the output terminals. Calculate the approximate time taken for the output voltage to reach 0 V after the 9 V supply is switched off.


.....

(6 marks)



3 An npn junction transistor is to be used as a switch to control an electromagnetic relay.

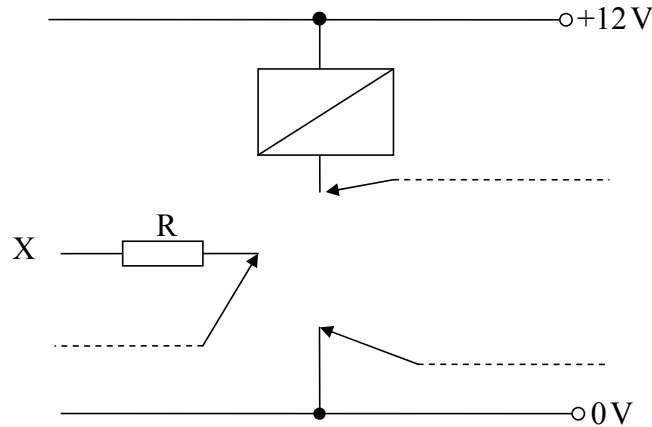- 3 (a) (i) Complete the circuit diagram to show how the transistor is connected, label the leads of the transistor in the spaces shown.



- 3 (a) (ii) Add to the diagram the component required to protect the transistor from the back emf of the relay.

(6 marks)

3 (b) The relay coil has a resistance of 240Ω .

- 3 (b) (i) Calculate the collector current of the transistor when the relay is switched on.

.....

.....

- 3 (b) (ii) The transistor has a current gain (ratio of collector current to base current) of 50. Calculate the minimum base current when the relay is switched on.

.....

.....

- 3 (b) (iii) The input voltage at X which saturates the transistor is 4.7V. Calculate the value of R, the resistor required.

.....

.....

- 3 (b) (iv) Choose the most appropriate value for R from the E24 series.

.....

(5 marks)

- 4 A student designs a very simple light level detector which indicates when the light level falls, as a reminder to switch on a reading lamp to avoid eye strain.

Since the detector is to be battery powered, it must have a **minimum** power consumption.

The following data is gathered about the devices that could be used.

For the input sensor:

LDR type	resistance at 10 lux
a	200 k Ω
b	94 k Ω
c	20 k Ω

For the processing stage:

type	relevant information
NOT gate 4049	Power consumption 0.001 mW
op-amp TL081	Supply current 1.4 mA
op-amp 741	Supply current 1.7 mA

For the output stage:

device	relevant information
filament lamp	6 V 0.06 A
red LED	V_f 2V @ 10 mA

- 4 (a) Choosing from the tables above, select a suitable device and type for each of the subsystems that would result in the lowest current drawn from the battery. Label the system diagram with them.



(3 marks)

- 4 (b) The system could be designed to indicate low light by either switching the output device on or off. Which would be better? Give your reason.

.....

.....

(2 marks)



- 4 (c) The LDR has a resistance of $150\text{ k}\Omega$ at the light level at which the system should alert the user. The chosen processing stage requires an input voltage of 4.5 V to switch. Draw the circuit diagram of a voltage divider that would give a rising voltage as the light level falls marking the output connection and suitable value for the component other than the LDR.

_____ ○ $+9\text{ V}$

_____ ○ 0 V

(3 marks)

- 4 (d) The output of the process stage is 7.3 V , and the minimum output current that will operate the output device is 3 mA at 1.9 V .

Calculate the value of a series resistor for the output device.

.....

.....

(2 marks)

Turn over for the next question



5 A student designs a noise warning system to alert the user to the presence of a noise level likely to damage hearing. An LED flashes on and off when the noise level exceeds a safe value.

5 (a) Label each subsystem in the system diagram below to show a possible design for the noise warning system using the following subsystems:


NOR gate

astable

comparator

LED

sound sensor

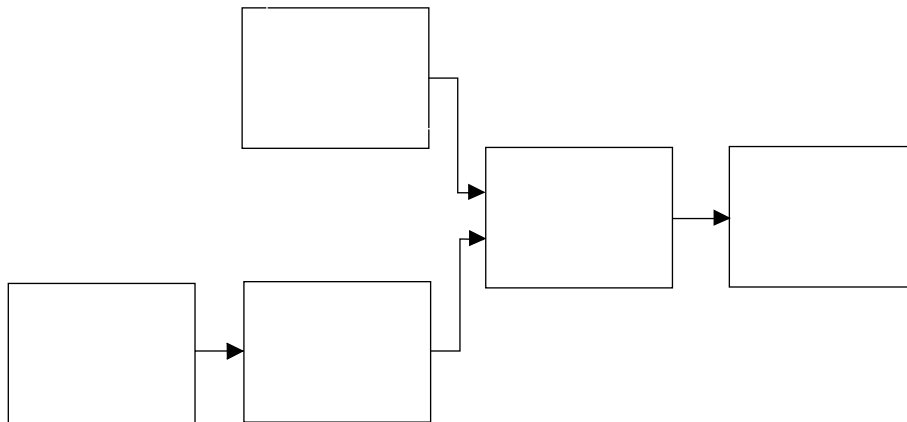

(5 marks)


5 (b) In which subsystem could

5 (b) (i) an op-amp be used.....

5 (b) (ii) a 555 IC be used?.....

(2 marks)

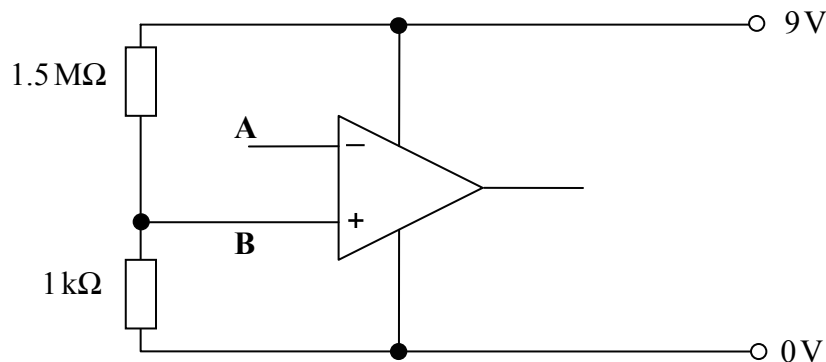5 (c) The comparator circuit diagram is shown below.



- 5 (c) (i) Calculate the voltage at point **B** in this circuit

.....

.....

The signal from the sound sensor is connected to point **A** in the comparator circuit. What voltage would you expect from the output of this circuit when


- 5 (c) (ii) the voltage at **A** is 4 mV

- 5 (c) (iii) the voltage at **A** rises to 10 mV?

(4 marks)

- 5 (d) Part of the astable circuit diagram is shown below.

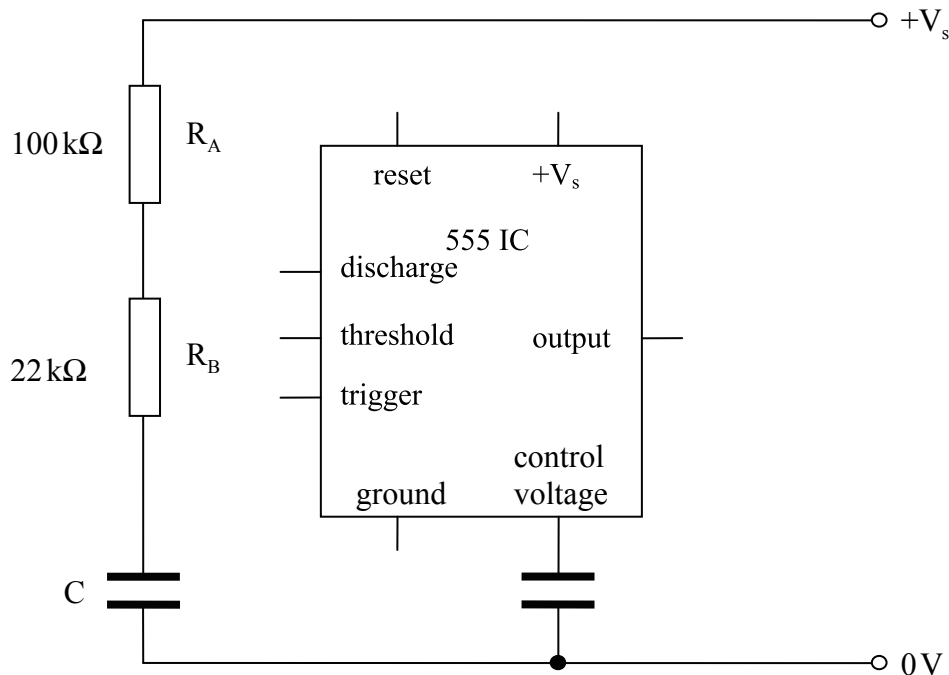- 5 (d) (i) Complete the circuit by drawing in the wire links required.



- 5 (d) (ii) Given the values shown on the circuit diagram for R_A and R_B , calculate the value of C required to give an output frequency of 2 Hz.

.....

.....

.....

(7 marks)

6 A zener diode is used to regulate the output voltage of a power supply to 5.1 V when an input voltage between 7 V and 9.6 V is applied.

6 (a) Add a zener diode and its current limiting resistor to complete the circuit diagram below.



(4 marks)

6 (b) The minimum zener current should be 5 mA under all conditions.
The maximum output current required is 60 mA.

6 (b) (i) Calculate the minimum voltage across the resistor.

.....

6 (b) (ii) What current flows through the resistor when the output current is 60 mA?

.....

6 (b) (iii) Calculate the required resistor value.

.....

6 (b) (iv) Which preferred E24 resistor value should be chosen?

.....

6 (b) (v) Calculate the power dissipated by the resistor when the input voltage is 9.6 V and the output current is 60 mA.

.....

.....

6 (b) (vi) Explain whether a 0.25 W power rating would be suitable for the resistor.

.....

(8 marks)

END OF QUESTIONS