



ASSESSMENT and
QUALIFICATIONS
ALLIANCE

Mark scheme

June 2003

GCE

Electronics


Unit ELE4

Copyright © 2003 AQA and its licensors. All rights reserved.

ELE4 – Electronic Control Systems


- 1**
- (a) (i) data in ROM cannot be changed, data in RAM can be ✓
ROM retains data after power is removed, Ram loses data ✓ etc.
max (1 mark)
- (ii) basic input and output instructions ✓
basic operating system commands ✓
any sensible response
(2 marks)
- (b) (i) A bus is a collection of wires along which data is sent and received and to which each section of the microcomputer system is connected ✓
(1 mark)
- (ii) Buses are used to reduce the number of connection routes needed ✓
(1 mark)
- (iii) To enable data to pass to and from the microprocessor (or RAM etc) ✓
(1 mark)
- (c) (i) Memory mapped ports are decoded as memory addresses and accessed as memory elements ✓
(1 mark)
- (ii) I/O mapping has its own separate control line (or commands) to indicate an address is an I/O port. ✓
I/O mapping does not take up memory allocation (addresses) ✓
(2 marks)
(Total 9)
- 2**
- (a) (i) a, b, c, d, g ✓
(1 mark)
- (ii) D_0, D_1, D_2, D_3 and D_6 ✓
i.e. 01001111 (or 79_{10}) ✓
giving 4F ✓
(3 marks)
- (b) (i) 60mA ✓
(1 mark)
- (ii) **5 LEDs** $\Rightarrow 5 \times 1.9 = 9.5V$ ✓
voltage across R approx. $15 - 9.5 = 5.5V$ ✓
 $\Rightarrow R = 5.5 / 0.06 = 91.7\Omega$ ✓
max (2 marks)
- (iii) **Power** $= V \times I = 5.5 \times 0.06$ ✓
 \Rightarrow **Power** $= 0.33W$ (accept 0.5 or 1W) ✓
(2 marks)
(Total 9)

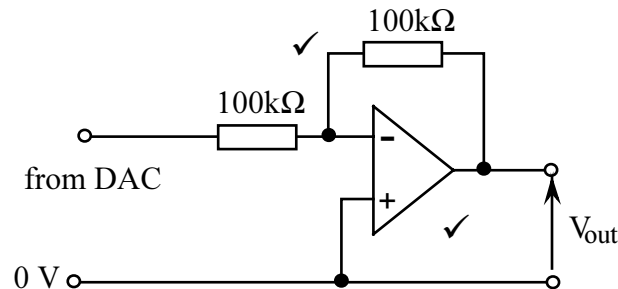- 3 (a) (i) Digital to Analogue Conversion ✓ (1 mark)
- (ii) $12.75\text{V} / 255$ ✓
 \Rightarrow change in output for a change of 1 in the input is 0.05V (50mV) ✓ (2 marks)
- (iii)



- (b) (i) **start:** is a label ✓ (2 marks)
- (ii) sends the integer variable N\% to the output port 378_{16} ✓ (1 mark)
- (c) Enter a number greater than 255 or less than 0 ✓ ✓ (1 mark)
- (2 marks)
(Total 9)

- 4 (a) (i)

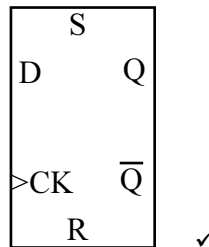

- (ii) whatever value is put on D is transferred to Q ✓
only on the rising edge of the clock pulse ✓ (1 mark)
- (b) (i) three possible output states ✓
0, 1, high impedance ✓ (2 marks)
- (ii) to isolate the outputs from the two 4 bit latches ✓ (2 marks)
- (c) (i) Neural networks have lots of very basic processors whereas a PC has a few complex processors ✓
data is stored through a neural network, whereas a PC stores it centrally ✓ (2 marks)
- (ii) justified reason e.g. No, because ANNs only predictive and are not able to do accurate measurements ✓ (1 mark)
- (Total 9)**

- 5 (a) (i) Whole system built in a single IC ✓
PICs have separate instruction bus ✓
(appropriate and sensible response) max (1 mark)
- (ii) Sensible answer e.g. cheap and very versatile ✓ (1 mark)

- (b) Closed loop when system monitors the output and uses state of output to control the input (feedback) ✓ eg.
Filling with water requires the amount of water to be monitored and stopped at the required amount - could not do by time because of variation in water pressure ✓
Heating could not be done by time because of variation in input water temp ✓
max (2 marks)
- (c) (i) Negative feedback is where information from the output is used to adjust the input so that the output remains steady ✓
(1 mark)
- (ii) If the speed is too fast the input drive to the motor will be reduced and vice versa if the speed is too slow ✓
(1 mark)
- (d) (i) thermistor ✓
(1 mark)
- (ii) thermistor is part of a voltage divider circuit which produces a voltage dependent upon the temperature of the thermistor. ✓
The op-amp compares this voltage with that from the PIC/AVR and produces a low output when the voltage from the voltage divider exceeds that from the PIC/AVR ✓
(2 marks)
- (Total 9)**
- 6 (a) To clean up the pulses,(restoring the logic levels and sharp rise and fall times) ✓
(1 mark)
- (b) (i) When the output is at 0V, the voltage divider connected to point A consists of a $47k\Omega$ resistor at the top and two $47k\Omega$ resistors in parallel at the bottom ✓
Combined resistance at bottom is $23.5k\Omega$ ✓
Voltage divided into ratio of 2:1 => voltage at point A = 4V ✓
(3 marks)
- (ii) When output is 12V, there are two $47k\Omega$ resistors at the top of the voltage divider and one $47k\Omega$ resistor at the bottom ✓
Combined resistance at top is $23.5k\Omega$ ✓
Voltage divided into ratio of 1:2 => voltage at point A = 8V ✓
(3 marks)
- (iii) Op-amp has a very large open loop voltage gain so acts as a comparator ✓
When the input rises above 8V, the inverting input to the op-amp is greater than the non-inverting input, so the output goes to 0V ✓
Similarly when the input voltage goes below 4V when the output is at 12V ✓
max (2 marks)
- (Total 9)**
- 7 (a) MOSFET or transistor with coils in drain/collector circuit. ✓
Input to gate or base (with series resistor) ✓
Protection diode for MOSFET/transistor correctly placed ✓
(3 marks)
- (b) (i) A 4 pole stepper motor rotates 7.5° as each successive coil is energised, so with four coils energised in sequence it rotates 30° ✓
(1 mark)
- (ii) Reverse the sequence ✓
so that D_3 is energised first, then D_2 , then D_1 then finally D_0 ✓
(2 marks)
- (iii) Alter the value of the **pause** ✓
(1 mark)

- (c) (i) **OUT(&H378)**, is command to write what follows to the parallel port and 4 corresponds to making the bit D₂ logic 1 ✓
(1 mark)
- (ii) **OUT(&H378), 1**
GOSUB waitabit
OUT(&H378), 2
GOSUB waitabit
OUT(&H378), 4
GOSUB waitabit
OUT(&H378), 8
STOP ✓ ✓ ✓ ✓
(4 marks)
- (d) (i) Polled is when the computer monitors a port by regularly reading its value ✓
(1 mark)
- (ii) Interrupt; the computer performs other operations until an external device generates a signal, upon which the computer will stop what it is doing and service the interrupting device. It does not therefore need to continuously monitor the device unlike with polling. ✓
(1 mark)
- (iii) Make the motor rotate one step at a time ✓
Read in the value of port (&H379) and examine bit 5 ✓
Repeat this until bit 5 is high, tube A is then aligned with the pipe ✓
(3 marks)
- (e) It would be very difficult to make a conventional motor accurately rotate 30° ✓
(1 mark)
(Total 18)

(Paper Total 72 marks)